

Control Systems

G V V Sharma*

CONTENTS

1 Feedback Circuits 1

Abstract—The objective of this manual is to introduce control system design at an elementary level.

Download python codes using

```
svn co https://github.com/gadepall/school/trunk/
control/codes
```

Output resistance without feedback is $10k\Omega$
Output resistance without feedback is greater than with feedback.

The following code generates the values

```
codes/ee18btech11042.py
```

1 FEEDBACK CIRCUITS

- 1.0.1. For a particular amplifier connected in a feedback loop in which the output voltage is sampled, measurement of the output resistance before and after the loop is connected shows a change by a factor of 100. Is the resistance with feedback higher or lower? What is the value of the loop gain GH ? If R_{of} is 100Ω , what is R_o without feedback.

Solution: We know that,

$$R_o = R_{of}(1 + GH) \quad (1.0.1.1)$$

Output resistance before and after the loop is connected changes by a factor 100. So,

$$100 = 1 + GH \quad (1.0.1.2)$$

$$GH = 99 \quad (1.0.1.3)$$

Open loop gain GH is 99.
Given,

$$R_{of} = 100 \quad (1.0.1.4)$$

$$R_o = 100(1 + 99) \quad (1.0.1.5)$$

$$R_o = 10000 \quad (1.0.1.6)$$

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.